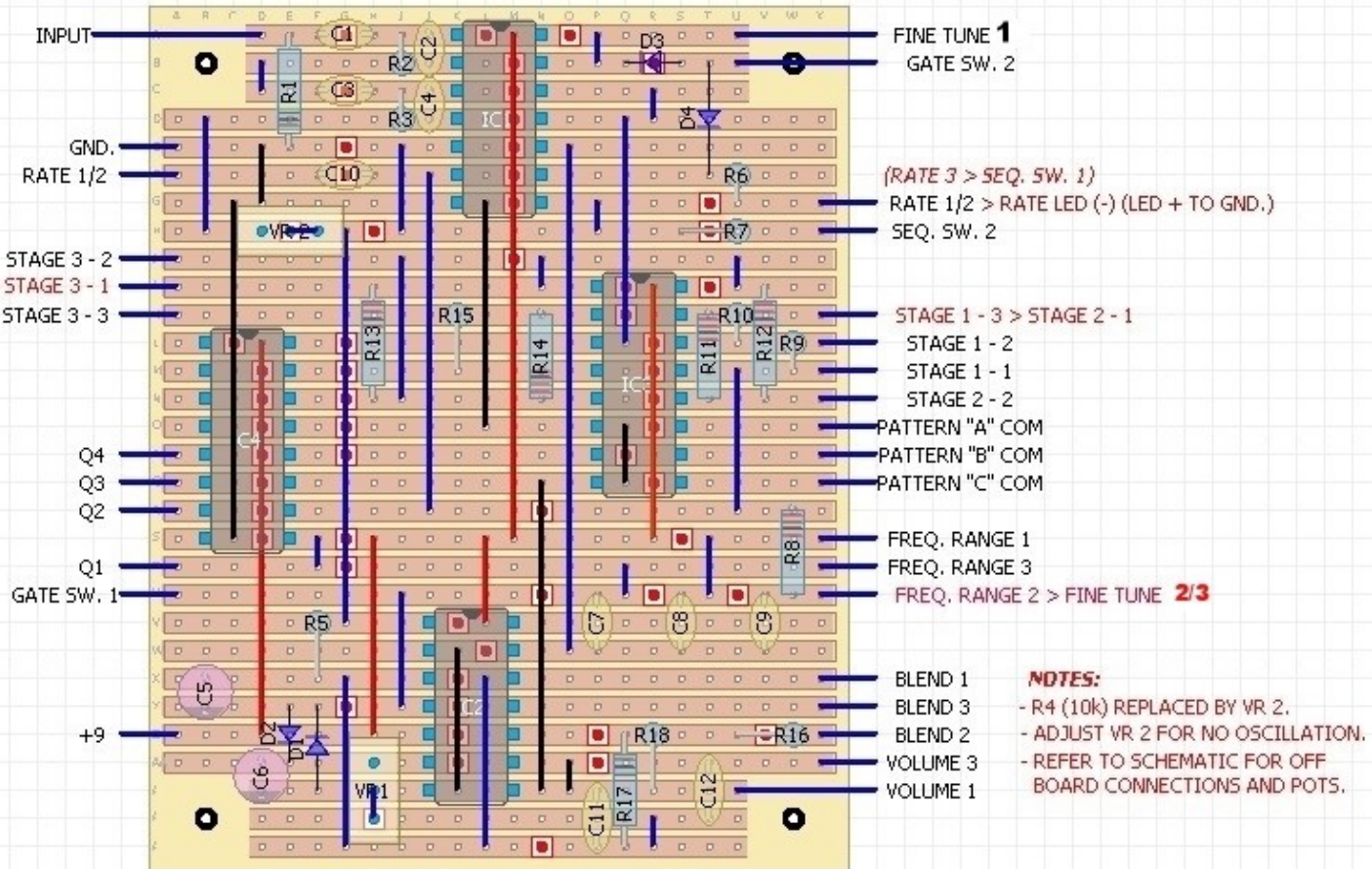


CORRUPTOR RING MODULATOR DESIGN: FREPPO LAYOUT: DIGI2T
59 CUTS - 33 JUMPERS **VERIFIED** 09 FEB. 2015



Veroboard
 C1, C3
 C2, C4, C11
 C5
 C6
 C7
 C8, C9
 C10
 C12
 D1, D2, D3, D4

24H x 30R
 100nF 63V
 2.2nF 63V
 2.2uF 50V
 1uF 50V
 33nF 63V
 10nF 63V
 220nF 63V
 1uF 63V
 1N4148

IC1
 IC2
 IC3
 IC4
 R1, R2, R3, R5
 R6, R7
 R8, R9, R10, R11, R12, R13, R14, R15
 R16
 R17, R18
 VR1, VR 2

CD4069
 CD4070
 CD4051
 CD4040
 1M
 10K
 22K
 22K 0.25W
 10K 0.25W
 100K Lin