



5K are multiturn trimmers. Adjust for +/- 17v

The 48v output only went up to around 42v on my build. It's enough for most condenser microphones.

Needs an AC/AC transformer with a center tap, that can supply at least 250mA (for two micre channels).

All diodes are 1N4007. Use capacitors rated at 100v or higher. Build at your own risk!